



The University of Azad Jammu and Kashmir, Muzaffarabad

Department of Software Engineering

Name

Kamal Ali Akmal

Course Name	Computer Architecture and Logic Design
Submitted to	Engr. Sidra Rafique
Semester	2nd
Session	2024-2028
Roll No	2024-SE-38
Lab No	02

Procedure to Connect 7408 (AND Gate IC) in EWB

1. Open EWB Software

- Start **Electronic Workbench** on your computer.

2. Place the 7408 IC

- Click on **Place** → **Component**.
- Go to the **TTL** or **Digital** library.
- Search and select **7408** (it's the Quad 2-input AND gate).
- Place the 7408 IC onto the workspace.

3. Connect the Power Supply

- **Pin 14**: Connect it to **+5V** (power supply).
- **Pin 7**: Connect it to **Ground (GND)**.

This powers up the IC so it works properly.

4. Set up Inputs

- From **Inputs** menu, pick **Logic Switches**.
- Place **two switches** (one for each input).
- Connect:
 - One switch to **Pin 1** (Input A1).
 - One switch to **Pin 2** (Input B1).

5. Set up Output

- From **Indicators** menu, place an **LED**.
- Put a **330Ω resistor** in series with the LED (protects the LED).
- Connect:
 - **Pin 3** (Output Y1) → Resistor → LED → Ground.

6. Start Simulation

- Click **Run** (or Start Simulation button).


7. Test the Circuit

- Use the switches to turn inputs ON or OFF.


- Observe the LED:
 - LED **ON** = Output is HIGH (1).
 - LED **OFF** = Output is LOW (0).
- Try all combinations (00, 01, 10, 11) and record the results.

AND GATE

Truth Table

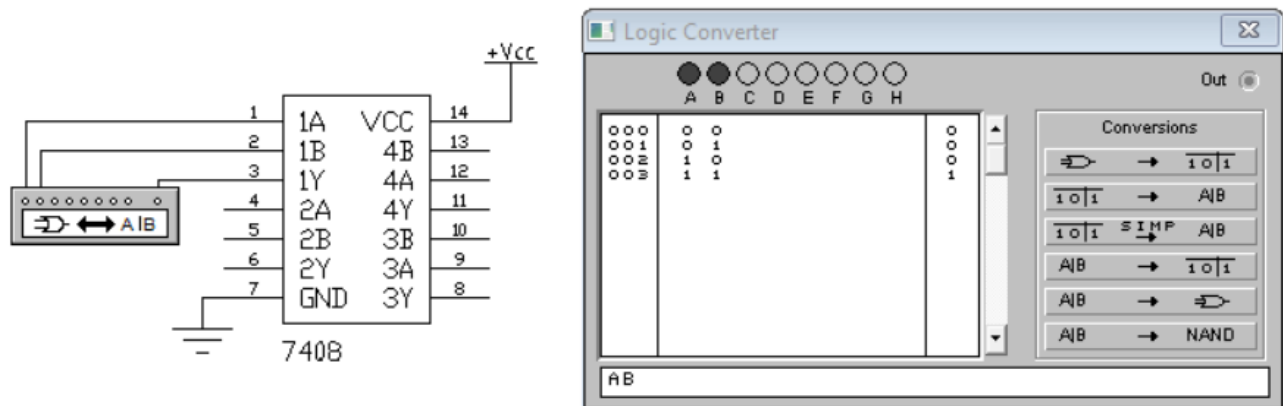

Output

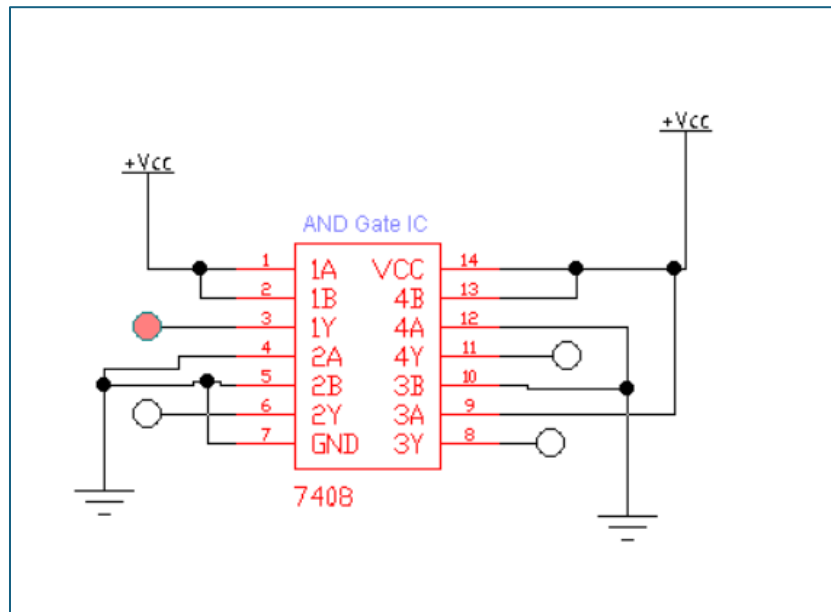

Procedure to Connect 7432 (OR Gate IC) in EWB

1. Open EWB Software

- Start **Electronic Workbench** on your computer.

2. Place the 7432 IC

- Click **Place** → **Component**.
- Find the **TTL** or **Digital** family.
- Search for **7432** (Quad 2-input OR gates).
- Place the **7432 IC** on your workspace.

3. Connect Power to the IC

- **Pin 14**: Connect to **+5V** (positive supply).
- **Pin 7**: Connect to **Ground (GND)**.

✂ This step powers the IC so it can work correctly during simulation.

4. Set Up Inputs

- From the **Inputs** menu, place **two logic switches**.
- Connect:
 - First switch to **Pin 1** (Input A1).
 - Second switch to **Pin 2** (Input B1).

5. Set Up Output

- From the **Indicators** menu, place an **LED**.
- Add a **330Ω resistor** between the output and the LED.
- Connect:
 - **Pin 3** (Output Y1) → **Resistor** → **LED** → **Ground**.

6. Start the Simulation

- Click **Run** to start the simulation.


7. Test and Observe

- Toggle the switches through different combinations (00, 01, 10, 11).
- Watch the LED:


- LED **ON** = Output is HIGH (1).
- LED **OFF** = Output is LOW (0).
- Record the output to make your **truth table**.

OR GATE

Truth table

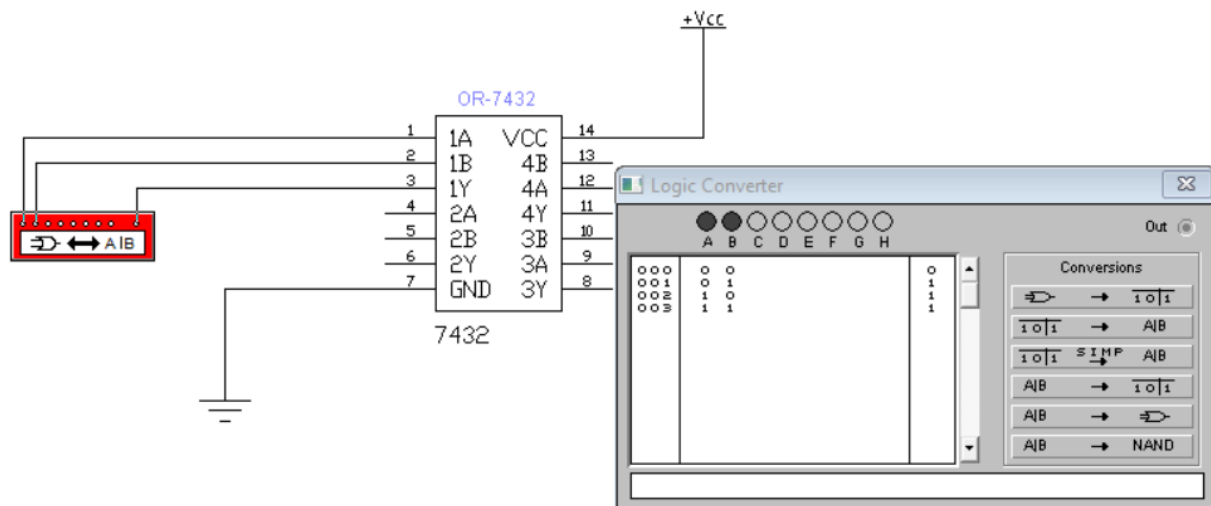

Output

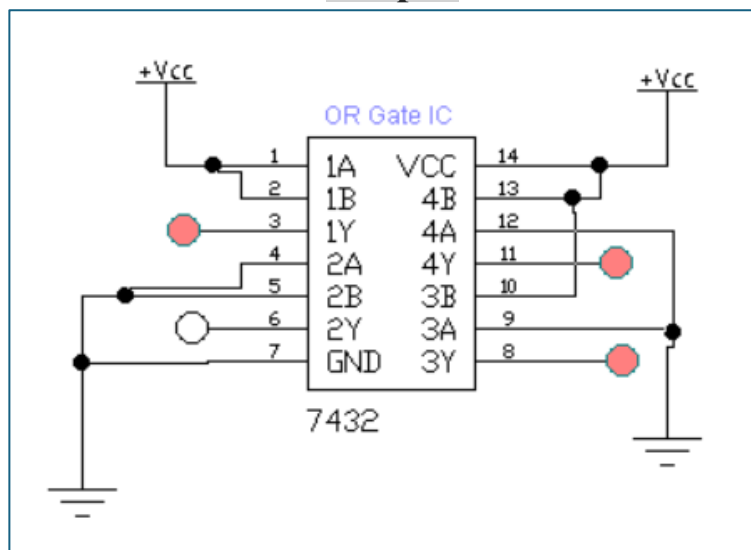

Procedure to Connect 7400 (NAND Gate IC) in EWB

1. Open EWB Software

- Start **Electronic Workbench** on your computer.

2. Place the 7400 IC

- Go to **Place** → **Component**.
- Find the **TTL** or **Digital** library.
- Search for **7400** (Quad 2-input NAND gate).
- Drag and place the IC on your workspace.

3. Connect Power to the IC

- **Pin 14**: Connect it to **+5V** (positive supply).
- **Pin 7**: Connect it to **Ground (GND)**.

✂ This powers up the IC so it works properly in the simulation.

4. Setup Input Connections

- From the **Inputs** menu, place **two logic switches**.
- Connect:
 - First switch to **Pin 1** (Input A1).
 - Second switch to **Pin 2** (Input B1).

5. Setup Output Connection

- From the **Indicators** menu, place an **LED**.
- Add a **330Ω resistor** in series with the LED.
- Connect:
 - **Pin 3** (Output Y1) → **Resistor** → **LED** → **Ground**.

6. Start the Simulation


- Press the **Run** button to start the simulation.

7. Test and Observe


- Turn ON and OFF the switches in different combinations (00, 01, 10, 11).
- Watch the LED:
 - LED **ON** = Output is HIGH (1).
 - LED **OFF** = Output is LOW (0).
- Record the results for each combination to create the **truth table**.

NAND GATE

Truth table

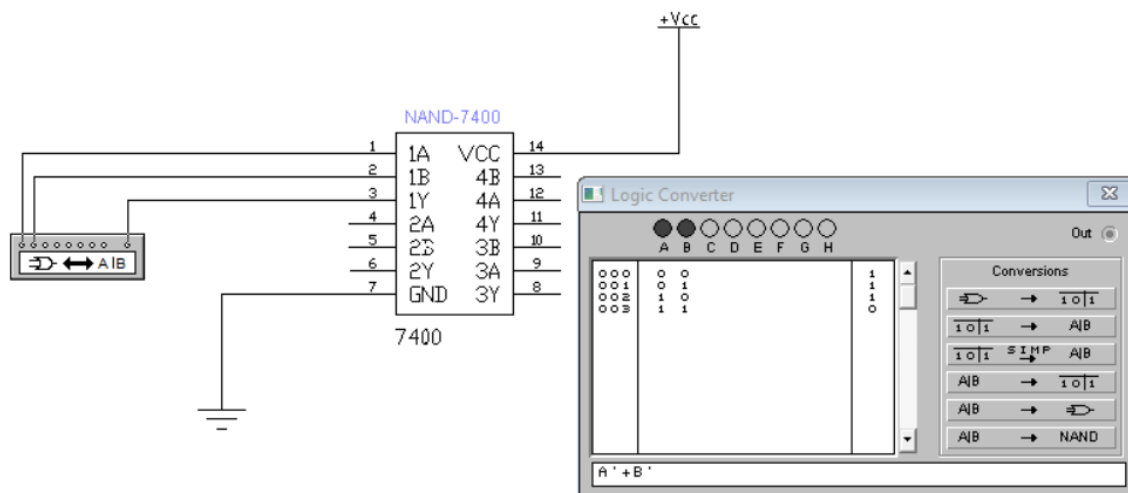

Output

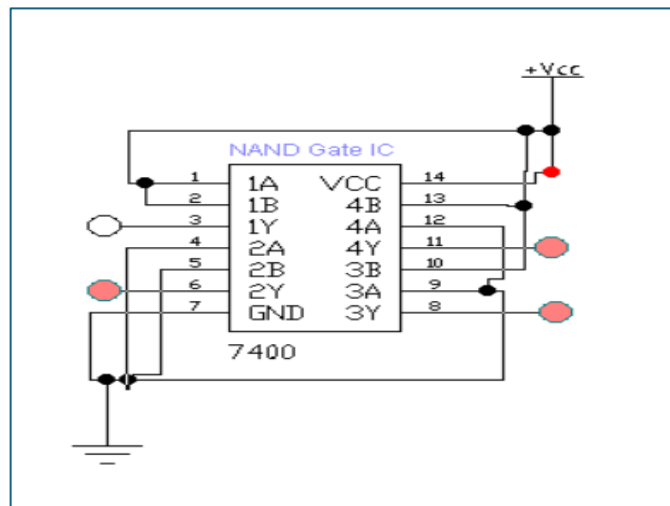

Procedure to Connect 7402 (NOR Gate IC) in EWB

1. Open EWB Software

- Start **Electronic Workbench** on your computer.

2. Place the 7402 IC

- Click **Place** → **Component**.
- Go to **TTL** or **Digital** library.
- Search for **7402** (Quad 2-input NOR gates).
- Place the **7402 IC** onto your workspace.

3. Connect Power to the IC

- **Pin 14**: Connect to **+5V** (positive power supply).
- **Pin 7**: Connect to **Ground (GND)**.

⚡ Powering the IC is necessary to make it work properly.

4. Set Up Inputs

- From the **Inputs** section, place **two logic switches**.
- Connect:
 - First switch to **Pin 1** (Input A1).
 - Second switch to **Pin 2** (Input B1).

5. Set Up Output

- From the **Indicators** section, place an **LED**.
- Add a **330Ω resistor** between the output and LED.
- Connect:
 - **Pin 3** (Output Y1) → **Resistor** → **LED** → **Ground**.

6. Start the Simulation

- Click **Run** to start the simulation.


7. Test and Observe

- Change the switches to different combinations (00, 01, 10, 11).
- Watch the LED:


- LED **ON** = Output is HIGH (1).
- LED **OFF** = Output is LOW (0).
- Write down the results to create the **truth table**.

NOR GATE

Truth table

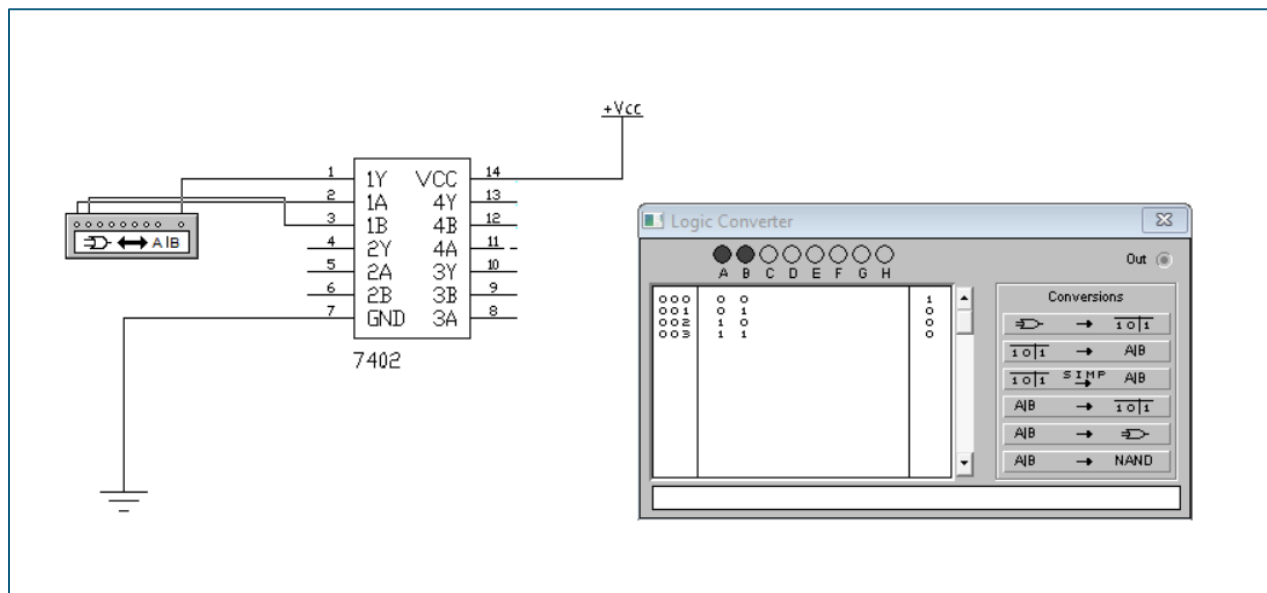

Output

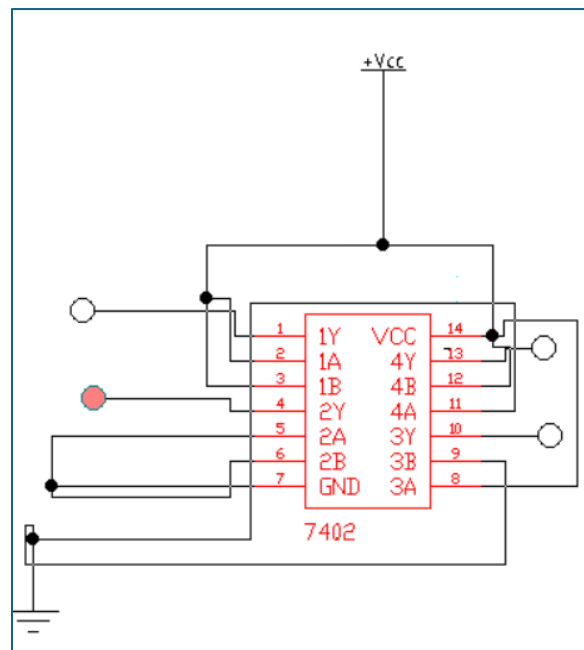

Procedure to Connect 7404 (NOT Gate/Inverter IC) in EWB

1. Open EWB Software

- Start **Electronic Workbench** on your computer

2. Place the 7404 IC

- Click on **Place** → **Component**.
- Find the **TTL** or **Digital** library.
- Search for **7404** (Hex Inverter/NOT gates).
- Place the **7404 IC** onto your workspace.

3. Connect Power to the IC

- **Pin 14**: Connect to **+5V** (positive power).
- **Pin 7**: Connect to **Ground (GND)**.

✂ This step powers the IC so it works properly.

4. Set Up Input

- From the **Inputs** menu, place **one logic switch**.
- Connect the switch to **Pin 1** (Input A1).

5. Set Up Output

- From the **Indicators** menu, place an **LED**.
- Add a **330Ω resistor** between the output and LED.
- Connect:
 - **Pin 2** (Output Y1) → **Resistor** → **LED** → **Ground**.

6. Start the Simulation


- Click **Run** to start simulation.

7. Test and Observe


- Turn the switch ON and OFF (0 or 1).
- Observe the LED:
 - If input is **0** → LED turns **ON** (Output 1).
 - If input is **1** → LED turns **OFF** (Output 0).

NOT GATE

Truth table

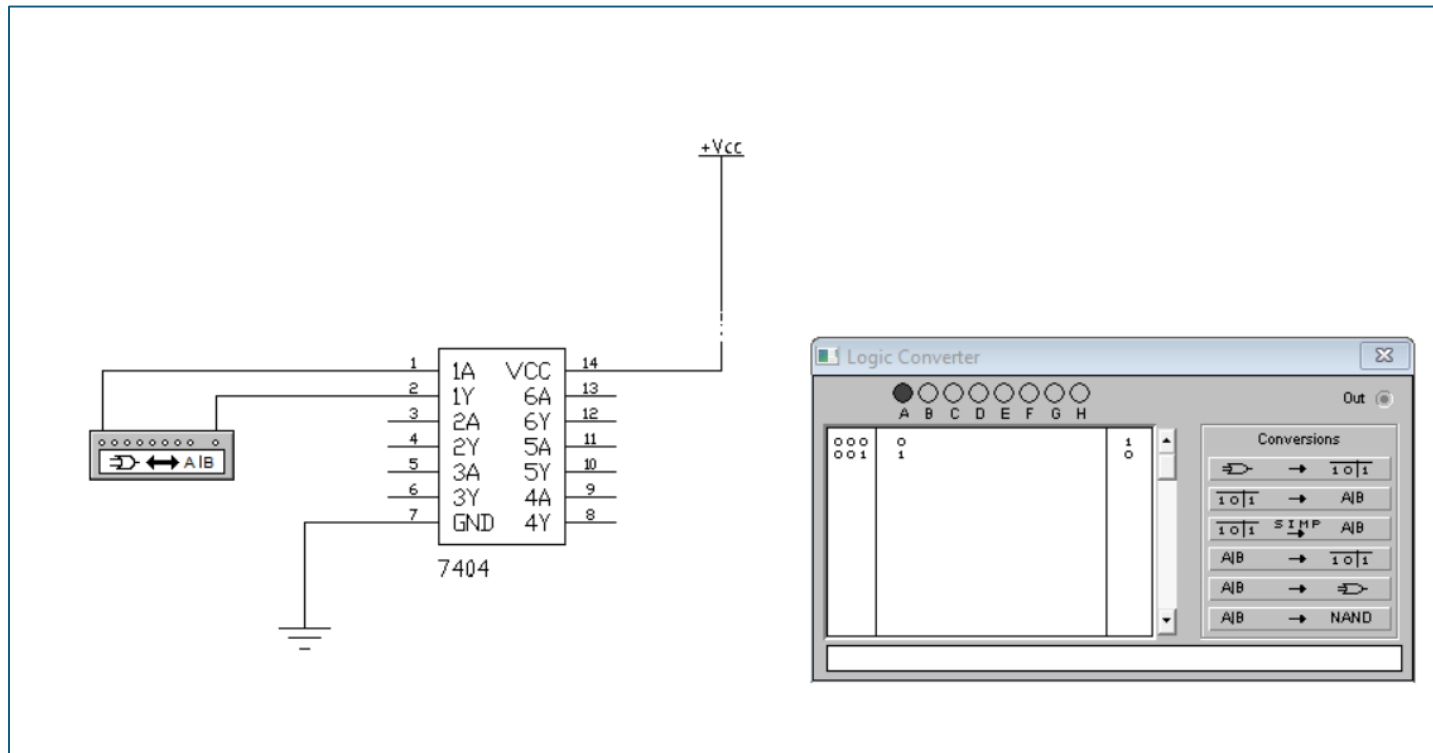

Output

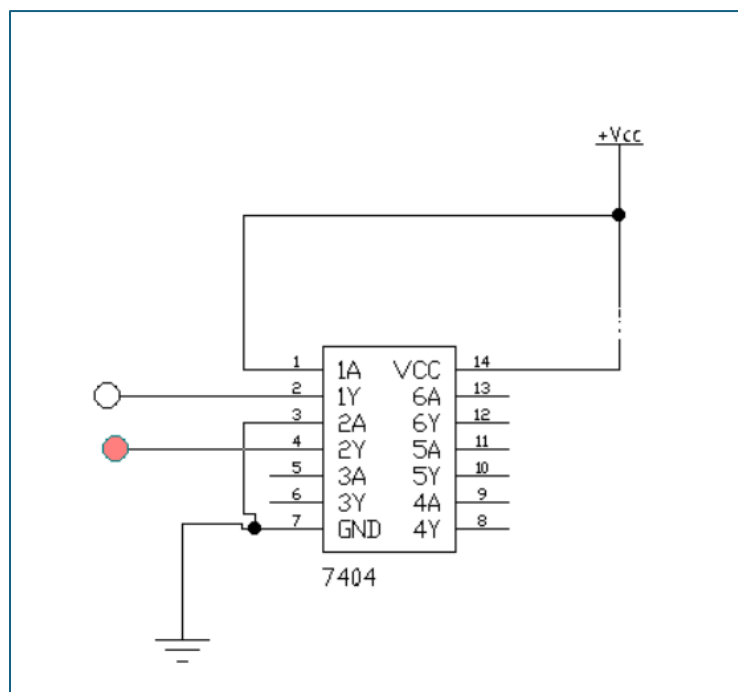

Procedure to Connect 7486 (XOR Gate IC) in EWB

1. Open EWB Software

- Launch **Electronic Workbench** on your computer.

2. Place the 7486 IC

- Go to **Place** → **Component**.
- Find the **TTL** or **Digital** section.
- Search for **7486** (Quad 2-input XOR gates).
- Drag and place the **7486 IC** onto your workspace.

3. Connect Power to the IC

- **Pin 14**: Connect to **+5V** (positive supply).
- **Pin 7**: Connect to **Ground (GND)**.

✂ This is needed to power the IC so it works during simulation.

4. Set Up Inputs

- From the **Inputs** menu, place **two logic switches**.
- Connect:
 - One switch to **Pin 1** (Input A1).
 - One switch to **Pin 2** (Input B1).

5. Set Up Output

- From the **Indicators** menu, place an **LED**.
- Add a **330Ω resistor** in series with the LED.
- Connect:
 - **Pin 3** (Output Y1) → **Resistor** → **LED** → **Ground**.

6. Start the Simulation

- Click the **Run** button to begin simulation.


7. Test and Observe

- Use the switches to test all input combinations (00, 01, 10, 11).
- Observe the LED:

- LED **ON** = Output is HIGH (1).
- LED **OFF** = Output is LOW (0).
- Record results to build the **truth table**s

XOR GATE

Truth table

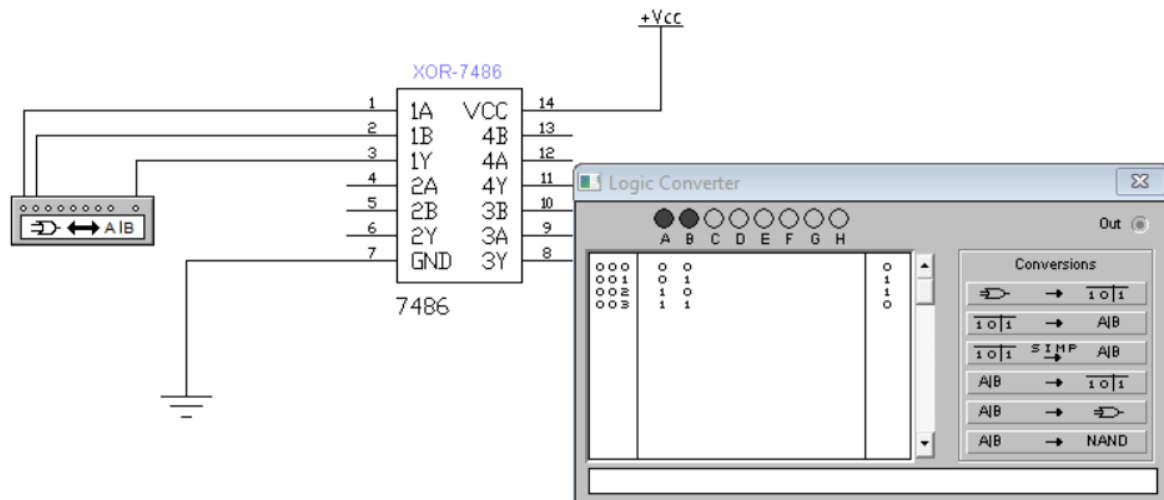

Output

