



# The University of Azad Jammu and Kashmir, Muzaffarabad

Name	Kamal Ali Akmal Jawahir Ali Raja Afzaal Ajmal Syed Ahmed Gillani
Group No	06
Session	2024-2028
Instructor	Engr. Sidra Rafique
Subject	Computer Architecture & Logic Design
Project Topic	Fire Alarm System

## Lab Report: Fire Alarm System

---

### Objective



The objective of this experiment was to design and implement a basic **fire alarm system** using simple electronic components. The system is intended to detect smoke or fire and immediately alert through a buzzer.

---

### Apparatus / Components Used

- **Battery (DC 9V / 12V)** – to provide power supply.
  - **Breadboard** – for building the circuit without soldering.
  - **IR Sensor** – to detect fire or flame by sensing infrared radiation.
  - **Smoke Detector Sensor (MQ-2/MQ-135)** – to detect smoke in the environment.
  - **Buzzer** – for audio alarm output.
  - **Switch** – to turn the system ON/OFF.
  - **Connecting Wires** – to establish connections between components.
-

## Circuit Diagram

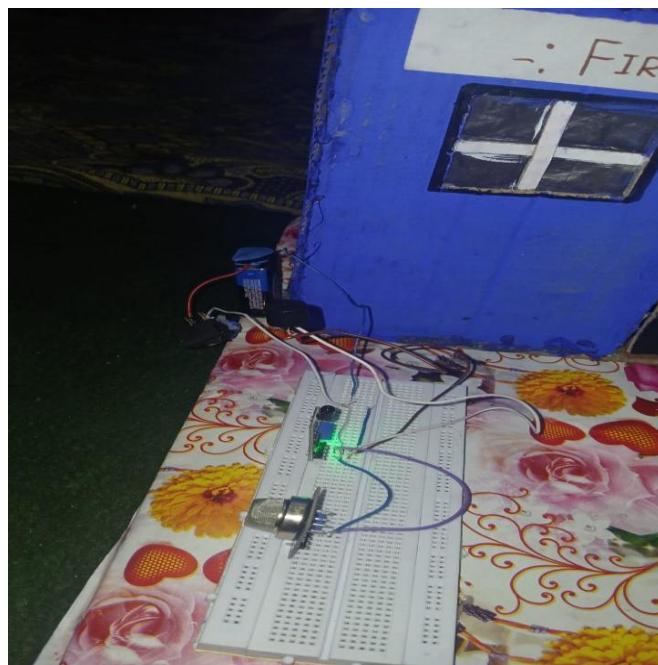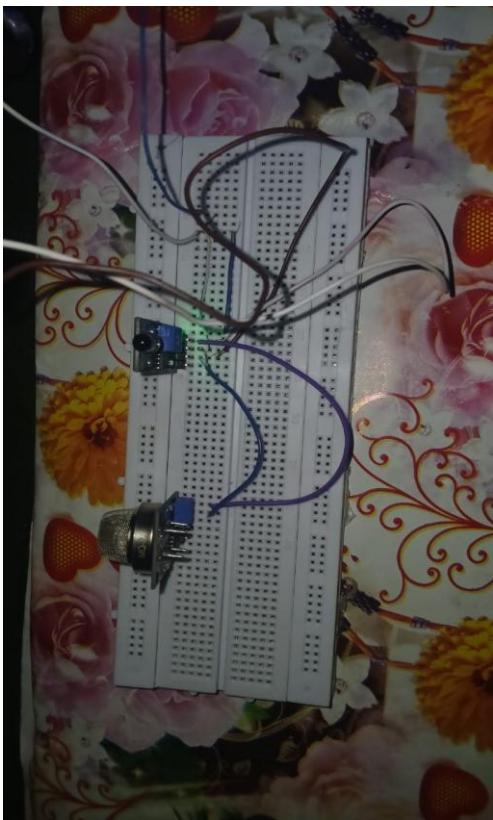

## Theory

A fire alarm system is designed to sense the presence of **fire indicators** (smoke, gas, or infrared light from flames). In this project:

- The **IR sensor** detects the heat/flame by sensing infrared radiation.
  - The **smoke detector** senses the concentration of smoke particles in the air.
  - If either sensor detects abnormal conditions, the circuit is triggered.
  - The **buzzer** produces a loud sound to alert nearby people.
  - The **switch** is used as a control to turn the system ON or OFF.
- 

## Procedure

1. Place all components on the **breadboard**.
  2. Connect the **battery** to the power rails of the breadboard.
  3. Connect the **switch** in series with the battery to control power.
  4. Attach the **IR sensor** and **smoke detector** outputs to the input pins of the buzzer circuit.
  5. Ensure the sensors share a **common ground** with the battery.
  6. Connect the **buzzer** to the output such that it receives current when a sensor detects fire/smoke.
  7. Connect all parts with **jumper wires** carefully.
  8. Power ON the circuit using the switch.
  9. Test the system by bringing smoke (e.g., from a matchstick) near the sensor and/or flame near the IR sensor.
- 

## Observations

- When no fire or smoke was present, the buzzer remained **OFF**.
- On detecting smoke, the smoke sensor output triggered the buzzer.

- On sensing flame/heat (infrared radiation), the IR sensor activated the buzzer.
  - The system responded immediately and produced a loud alarm.
- 

## Result

A **working fire alarm system** was successfully built and tested using a battery, IR sensor, smoke detector, switch, buzzer, and breadboard connections. The buzzer activated when smoke or fire was detected, proving the system can provide an early warning in case of fire hazards.

---

## Applications

- Home and office fire alarm systems.
  - Industrial safety monitoring.
  - Laboratories and storage areas with flammable materials.
- 

## Conclusion

The experiment demonstrated the successful design of a low-cost and effective **fire alarm system**. Using simple electronic components, the system was able to reliably detect fire or smoke and produce an alarm, showing the importance of electronics in safety applications.