



# The University of Azad Jammu and Kashmir, Muzaffarabad

<b>Name</b>	Kamal Ali Akmal
<b>Course Name</b>	Computer Architecture and Logic Design
<b>Submitted to</b>	Engr. Sidra Rafique
<b>Semester</b>	2nd
<b>Session</b>	2024-2028
<b>Roll No</b>	2024-SE-38
<b>Lab No</b>	06
<b>Submission date</b>	19 August 2025

## Encoders & Decoders

### Encoder

- An **encoder** is a device or circuit that **converts information from one form to another (usually into a coded form)**.
- It takes  **$2^n$  input lines** and gives an **n-bit binary output**.
- Example:
  - A **decimal-to-binary encoder** converts decimal input (like 0–9) into binary code.
  - If you press key “5” on a keypad, the encoder outputs 0101 (binary for 5).

**Purpose:** Reduce many input lines into fewer coded output lines.

**Example:** 8-to-3 Encoder

*Keyboard key pressed → binary code sent to computer.*


#### **Truth Table:**

D7	D6	D5	D4	D3	D2	D1	D0			C	B	A
0	0	0	0	0	0	0	1			0	0	0
0	0	0	0	0	0	1	0			0	0	1
0	0	0	0	0	1	0	0			0	1	0
0	0	0	0	1	0	0	0			0	1	1
0	0	0	1	0	0	0	0			1	0	0
0	0	1	0	0	0	0	0			1	0	1
0	1	0	0	0	0	0	0			1	1	0
1	0	0	0	0	0	0	0			1	1	1

**Output Expression: -**

$C = D4 + D5 + D6 + D7$
$B = D2 + D3 + D6 + D7$
$A = D1 + D3 + D5 + D7$

## Encoder Diagram using EWB

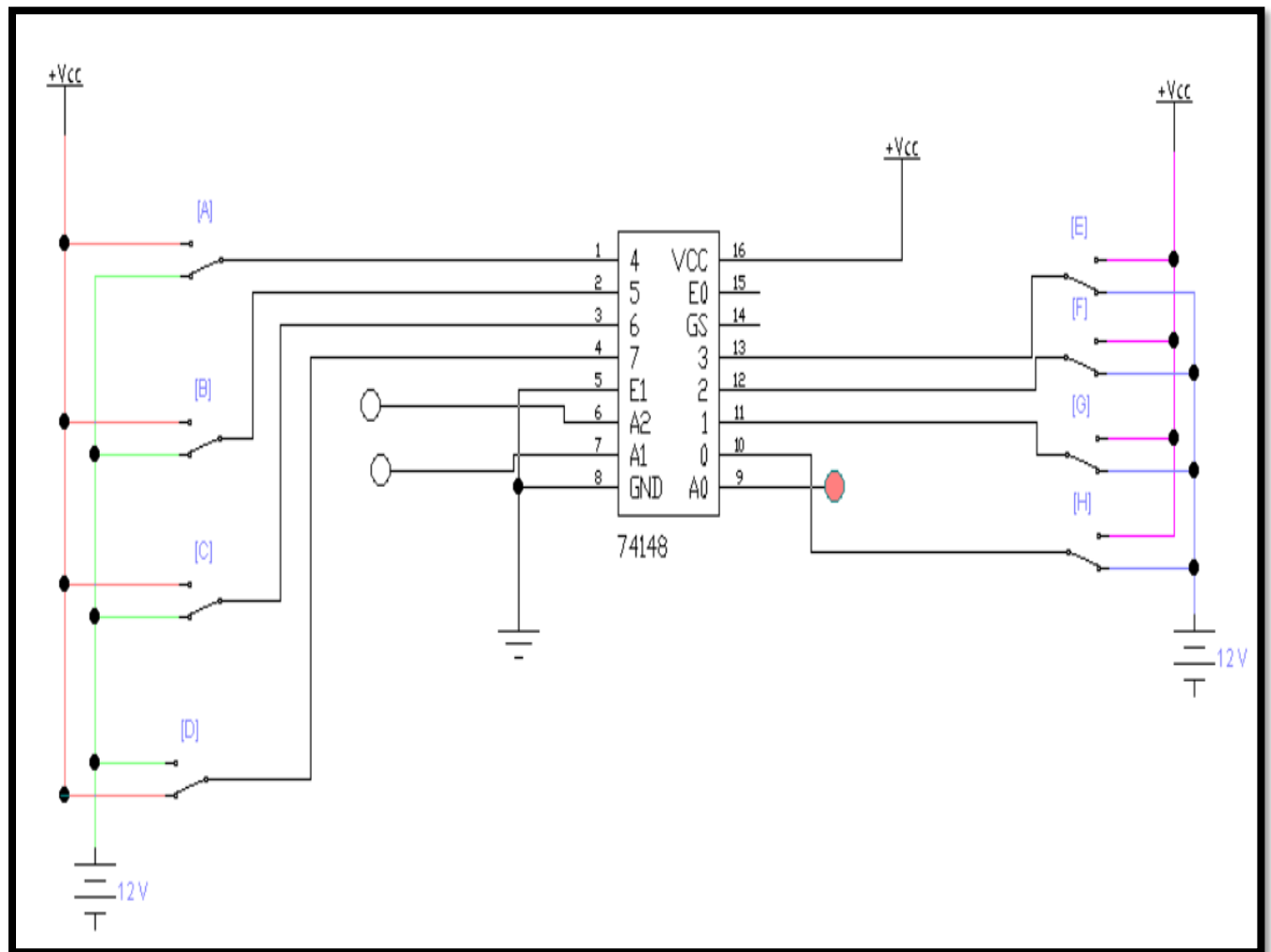

## Decoder

A decoder does the opposite of an encoder.

It takes **n-bit binary input and converts it into  $2^n$  outputs.**

### Example: 3-to-8 Decoder

A binary-to-decimal decoder takes binary 0101 and activates only output line 5.

Used in devices like 7-segment displays (to show numbers on digital clocks/calculators).

TV remote signal (binary) → decoded into commands (volume up, channel change).

**Purpose:** Expand coded input into its original unique output.

### Truth Table:

C	B	A	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

<i>Output Expressions</i>
$Y0 = EB'A'$
$Y1 = EB'A$
$Y2 = EBA'$
$Y3 = EBA$

## Decoder Diagram using EWB

